BEU CONNECT

Bihar Engineering University, Patna

B.Tech 4th Semester Exam., 2025

Code: 100403 | ***Time: 03 Hours***

Semester: IV | ***Subject: DIGITAL ELECTRONICS*** | ***Full Marks: 70***

Instructions:-

(i) The marks are indicated in the right-hand margin.
(ii) There are NINE questions in this paper.
(iii) Attempt FIVE questions in all.
(iv) Question No. 1 is compulsory.

Q.1 Choose the correct option / answer the following (Any seven question only): **[2 x 7 = 14]**

(a) A DAC with reference voltage 5 V and 8 bits has an LSB =……
(i) 19.5 mV (iii) 5 mV
(ii) 39 mV (iv) 0.78 mV

(b) A designer needs flexible logic. Best device
(i) PAL (iii) ROM
(ii) PLA (iv) FPGA

(c) A 1-bit memory can be implemented using
(i) 2 XOR gates (iii) 1 inverter
(ii) 2 NOR gates cross-coupled (iv) 3 OR gates

(d) RAM is
(i) Permanent (iii) Magnetic
(ii) Volatile (iv) Optical

(e) Which logic family has the lowest power consumption?
(i) TTL (iii) CMOS
(ii) ECL (iv) RTL

(f) BCD has how many valid binary combinations?
(i) 8 (iii) 10
(ii) 9 (iv) 12

(g) A Johnson counter with 5 FFs generates
(i) 5 states (iii) 8 states
(ii) 10 states (iv) 16 states

(h) The Boolean function F = Σm(0,2,4,6) corresponds to which simplified form?
(i) A′B′ (iii) A′
(ii) B′ (iv) A′C′

(i) Expanding memory size requires
(i) Adding ALUs (iii) Chip select logic
(ii) Decoder only (iv) Encoder only

(j) Tri-state logic provides
(i) High, Low, Open states (iii) Positive, Negative, Zero
(ii) High, Low, Negative (iv) High only

Q.2 **[7+7=14]**

(a) Design a counter with the following counting sequence: 0, 1, 3, 7, 6, 4, and repeat. Use T flip-flops.

BEU CONNECT
LEARN • GROW • SUCCEED
Your Engineering Journey, Simplified
PYQs • SYLLABUS • RESULTS
AI DOUBT SOLVER • ATTENDANCE • GATE MOCK TESTS
Free • Fast • Made by students
GET IT ON Google Play
Scan QR to download
Search BEU Connect on Play Store

(b) Describe the weighted-resistor DAC. Derive its output voltage equation

Q.3 **[7+7=14]**

(a) Design a full-subtractor with two half-subtractors and an OR gate.

(b) Simplify the Boolean function:
F = A′B′C′ + B′CD′ + A′BCD′ + AB′C′

Q.4 **[7+7=14]**

(a) Explain the structure and operation of Programmable Logic Arrays (PLA).

(b) Discuss the fabrication characteristics of CMOS devices. Explain why CMOS is preferred in modern VLSI systems.

Q.5 **[7+7=14]**

(a) Implement a full-adder circuit with a 3 × 8 decoder and two OR gates.

(b) Implement JK flip-flop using SR flip-flop.

Q.6 **[7+7=14]**

(a) Implement the Boolean function:
F = AB′CD′ + A′BCD + AB′C′D + A′BC′D
With exclusive-OR and AND gates.

(b) Describe the weighted-resistor DAC. Derive its output voltage equation.

Q.7 **[7+7=14]**

(a) Explain the internal working of the TTL NAND gate using a transistor-level diagram.

(b) Explain CCD (Charge Coupled Device) memory. Describe its operation and practical uses.

Q.8 **[7+7=14]**

(a) Implement the logic expression using a 4:1 mux variable. Assume variable AC as the select line
f(A,B,C) = Σm(1,2,3,5,6,7)

(b) Design a BCD- to-excess-3 code converter logic circuit.

Q.9 Write short note on any two of the following: **[7 x 2 = 14]**

(a) Explain the master-slave flip-flop operation.

(b) Compare JK, T, and D flip-flops.

(c) What is tri-state logic? Explain how it enables bus-oriented communication.

(d) Describe single-slope and dual-slope ADCs.

BEU CONNECT
LEARN • GROW • SUCCEED
Your Engineering Journey, Simplified
PYQs • SYLLABUS • RESULTS
AI DOUBT SOLVER • ATTENDANCE • GATE MOCK TESTS
Free • Fast • Made by students
GET IT ON Google Play
Scan QR to download
Search BEU Connect on Play Store